

MUKESH PATEL SCHOOL OF TECHNOLOGY MANAGEMENT AND ENGINEERING

(Affiliated to NMIMS Deemed to be University, Mumbai)



DIGITAL LOGIC DESIGN PROJECT

On

Priority Encoder

Submitted by

| | | |
|-----------------------|------|-------------|
| Reneeka Nadkarni | C034 | 70322000186 |
| Amishi Desai | C044 | 70322000023 |
| Chahel Gupta | C049 | 70322000047 |
| Semester/Year: IV/VII | | |

B. Tech Integrated Program

Department of Computer Science Engineering

MPSTME, Mumbai

2023-2024

PRIORITY ENCODER

INDEX

| Sr. No. | Description | Page No. |
|----------------|----------------------|-----------------|
| 1. | Introduction | 3 |
| 2. | Theory | 3 |
| 3. | Design & Principles | 4 |
| 4. | Simulation & Testing | 6 |
| 5. | Applications | 8 |
| 6. | Citations | 9 |

INTRODUCTION

An encoder has 2^n input lines and n output lines. The output lines create the binary code equivalent to the input value. So, a priority encoder is a circuit that executes the priority function. It is designed to efficiently manage a multitude of input lines (2^n) and transform them into a corresponding binary code on n output lines. In essence, it prioritizes the inputs based on their relative significance, ensuring that when multiple inputs are active simultaneously, the one with the highest priority takes precedence.

Understanding priority encoders is fundamental for comprehending advanced digital systems and forms the basis for optimizing various functionalities within electronic devices. This report delves into the foundational principles, design considerations, simulation, and applications of priority encoders, shedding light on its indispensable role in digital circuitry and its broad spectrum of real-world applications.

THEORY

To overcome the disadvantages of binary encoders, priority encoders were developed. We have $2^n : n$ priority encoder, but we will be focusing on 4:2 priority encoder.

4:2 Priority Encoder

4:2 priority encoder stands as a significant component within the family of encoders. With a capacity to handle four input lines and produce a two-bit binary output, this encoder is designed to discern and encode the highest priority active input among the available options.

The third output is 'E', which is considered as enable and it is set to 1 when more than one input line is high or active (1). If the enable bit is equal to '0', then all the inputs are '0'. In our case, the other 2 output lines are considered as don't care conditions denoted by 'X'.


Let's say D3, D2, D1, D0 are the inputs; Y1 and Y0 are the outputs and E is the enable bit indicator. Here, D3 input is the highest priority input and D0 is the lowest priority input. So, when the input D3 is active high (1), which has the highest priority irrespective of all other input lines, then the output of the 4-bit priority encoder is Y1(1) and Y2(1). When the D3 input is low and the D2 is high then D2 has the next highest priority irrespective of all other input lines, so the output is Y1(1) and Y2(0). Similarly, when D1/D0 will be active high and rest active low, the same will occur.

The simplified output expressions (Y1, Y2) can be obtained for a 4-bit encoder with the help of a Karnaugh map (K-map). From the output expressions, the 4:2 priority encoder circuit diagram is illustrated with logic gates.

The circuit diagram of 4:2 priority encoder is drawn with 2 OR gates, and the combination of AND gate and the NOT gate represent the enable bit, which is used when more than one input is logic high (1). Thus, four inputs with two outputs are encoded based on the assigned priority to the inputs.

DESIGN & PRINCIPLES

Symbol

 

Truth table

| Inputs | | | | Outputs | | |
|--------|----|----|----|---------|----|--------|
| D3 | D2 | D1 | D0 | Y1 | Y0 | Enable |
| 0 | 0 | 0 | 0 | X | X | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | X | 0 | 1 | 1 |
| 0 | 1 | X | X | 1 | 0 | 1 |
| 1 | X | X | X | 1 | 1 | 1 |

Expanded truth table (with don't care values)

| Inputs | | | | Outputs | | |
|--------|----|----|----|---------|----|--------|
| D3 | D2 | D1 | D0 | Y1 | Y0 | Enable |
| 0 | 0 | 0 | 0 | X | X | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 1 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 | 1 | 1 |

K-map for Y1

| D1 D0 \ D3 D2 | 00 | 01 | 11 | 10 |
|---------------|----|----|----|----|
| 00 | X | 1 | 1 | 1 |
| 01 | 0 | 1 | 1 | 1 |
| 11 | 0 | 1 | 1 | 1 |
| 10 | 0 | 1 | 1 | 1 |


$$\underline{Y1} = D3 + D2$$

K-map for Y0

| D1 D0 \ D3 D2 | 00 | 01 | 11 | 10 |
|---------------|----|----|----|----|
| 00 | X | 0 | 1 | 1 |
| 01 | 0 | 0 | 1 | 1 |
| 11 | 1 | 0 | 1 | 1 |
| 10 | 1 | 0 | 1 | 1 |

$$\underline{Y0} = D1.D2' + D3$$

Circuit Diagram

 

SIMULATION & TESTING



DLD Project - 4:2 Priority Encoder

<https://www.tinkercad.com/things/bm26KhEuhHY-copy-of-4-to-2-priority-encoder/editel?sharecode=e2S26zOZ6Lh441NYPSdu0KaVlgRUhMuK6xNZe8z0RIA>

Component List

| Name | Quantity | Component |
|------------|----------|-----------------------|
| P1 | 1 | 5, 5 Power Supply |
| U1 | 1 | Quad OR gate |
| U2 | 1 | Quad AND gate |
| U3 | 1 | Hex Inverter |
| R1, R2, R3 | 3 | 1 k Ω Resistor |
| D1, D3 | 2 | Red LED |
| D2 | 1 | Green LED |
| SW1 | 1 | DIP Switch SPST x 4 |

4:2 Priority Encoder

5.00 V
8.99 mA

D0 D1 D2 D3

ON

Y1 Y0 ENABLE

74HC32 74HC08 74HC04

DL D PROJECT
C034 Reneeka Nadkarni
C044 Amishi Desai
C049 Chahel Gupta

Simulator time: 00:00:09

The screenshot displays a Tinkercad circuit simulation for a 4:2 Priority Encoder. The circuit is built on a breadboard and includes the following components and connections:

- Power Supply:** A 5V DC source (P1) is connected to the VCC pins of the 74138 decoder (U3) and the 7401 NAND gate (U2). The GND pins of U3 and U2 are connected to the common ground.
- Decoder (U3):** A 74138 3-to-8 line decoder. Its three data inputs (A, B, C) are connected to the outputs of a 4-to-2 priority encoder (U1). The decoder's eight outputs (Y0-Y7) are connected to the inputs of a 4-to-2 priority encoder (U2).
- Encoder (U2):** A 7401 4-input NAND gate. Its four inputs are connected to the outputs of the 74138 decoder (U3). The output of U2 is connected to the output of the 4-to-2 priority encoder (U1).
- Encoder (U1):** A 7400 4-input NAND gate. Its four inputs are connected to the outputs of the 7401 NAND gate (U2). The output of U1 is connected to the output of the 4-to-2 priority encoder (U1).
- Switch (SW1):** A single-pole double-throw switch connected to the output of the 4-to-2 priority encoder (U1).
- Resistors:** Three 1kΩ resistors (R1, R2, R3) are used to pull up the inputs of the 7401 NAND gate (U2) and the 7400 NAND gate (U1) to the 5V supply.
- LEDs:** Two LEDs, D1 (RED) and D2 (GREEN), are connected to the outputs of the 4-to-2 priority encoder (U1) to provide visual feedback.

The circuit is titled "4:2 Priority Encoder" and is the first sheet of a two-sheet document.

APPLICATIONS

Priority encoders, fundamental components of digital circuits, find extensive applications across various domains due to their ability to efficiently manage and encode inputs based on predefined priority levels. Some applications include:

1. Interrupt Handling in Microprocessors

Priority encoders are used to manage interruptions in microprocessors, where various devices or processes may simultaneously request a service. It helps prioritize these requests, ensuring that the most critical tasks are addressed first.

2. Network Routing

In computer networks, includes devices such as routers and switches, priority encoders are employed to prioritize incoming data packets based on factors like quality of service, ensuring efficient data routing and allocation of network resources.

3. Traffic Light Control Systems

Priority encoders are also utilized in traffic light control systems to manage traffic flow. Different traffic lanes or routes are assigned priorities, allowing for the smooth movement of vehicles and pedestrians through intersections.

4. Real-time Systems

In real-time systems where immediate and time-critical responses are necessary, priority encoders help to manage multiple inputs/events, ensuring that the most critical tasks are processed first and within specified timeframes.

5. Data Compression and Encryption

Priority encoders optimise compression and encryption processes by assigning priorities to different data packets or segments based on their importance or characteristics.

CITATIONS

- Tanenbaum, A. S., & Van Steen, M. (2007). Distributed Systems: Principles and Paradigms. Pearson Education.
- Kurose, J. F., & Ross, K. W. (2017). Computer Networking: A Top-Down Approach. Pearson.
- Papadimitriou, D., & Pohl, E. A. (2013). Traffic Engineering and QoS Optimization of Integrated Voice & Data Networks. John Wiley & Sons.
- Ogata, K. (2010). Modern Control Engineering. Pearson Education.
- Liu, J., & Layland, J. W. (1973). Scheduling algorithms for multiprogramming in a hard-real-time environment. Journal of the ACM (JACM), 20(1), 46-61.
- Sayood, K. (2006). Introduction to Data Compression. Morgan Kaufmann.